
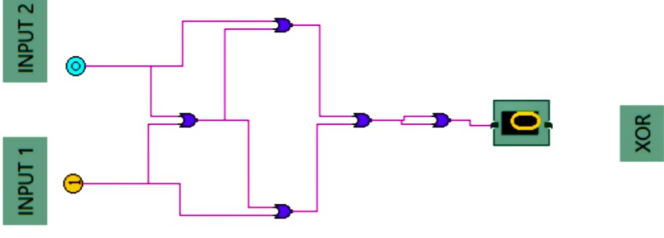
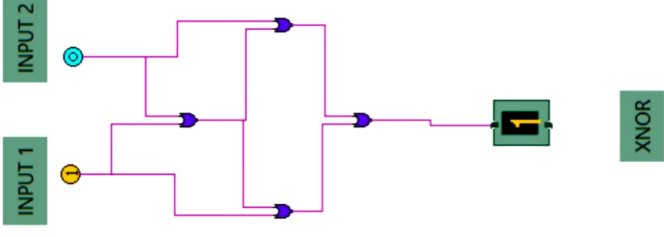
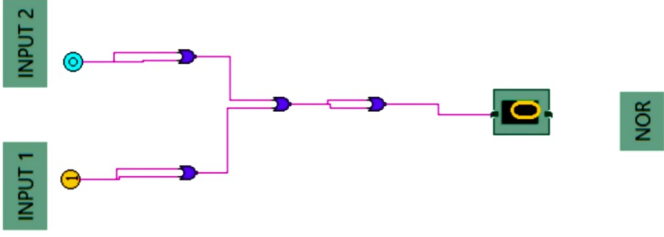
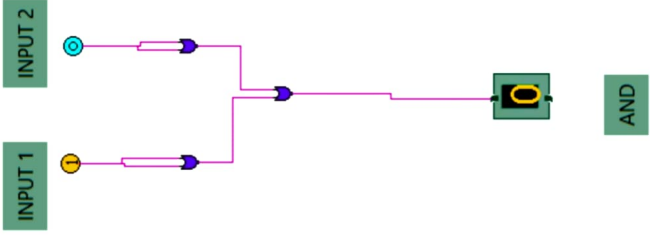


ALL LOGIC GATE USING UNIVERSAL NAND

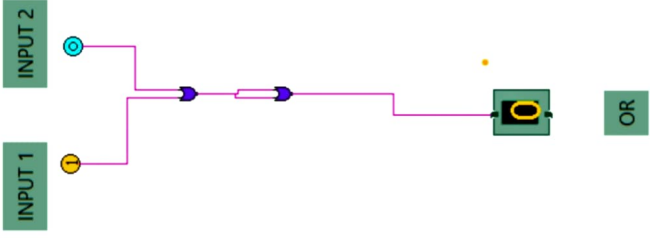

ALL LOGIC GATE USING UNIVERSAL NAND