

INPUT 1

INPUT 2



0

AND GATE



1

OR GATE



1

NOT GATE



1

NAND GATE



0

NOR GATE



1

XOR GATE



0

XNOR GATE

OUTPUT

ALL BASIC GATES